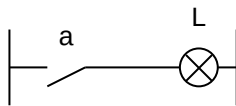
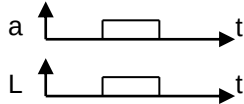
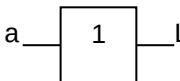
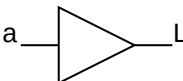
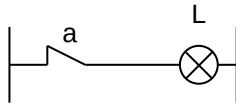
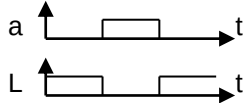
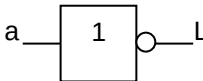
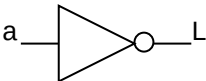
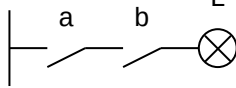
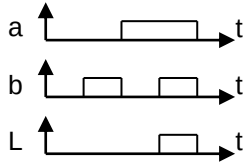
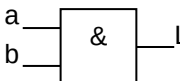
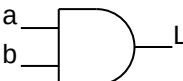
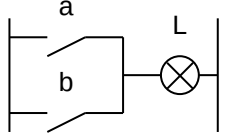
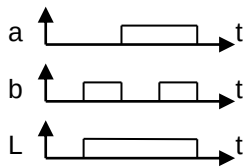
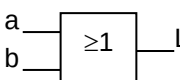
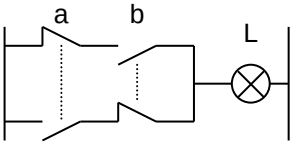
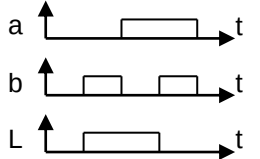
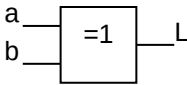
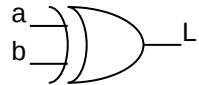
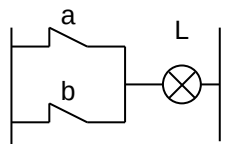
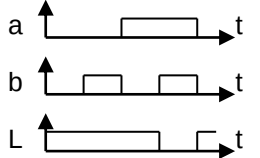
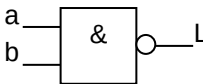
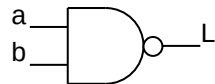
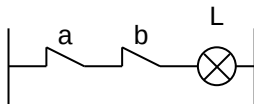
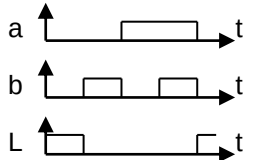
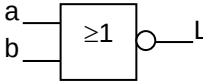
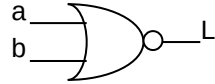
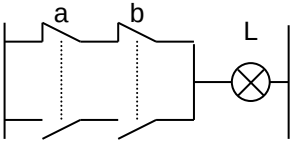
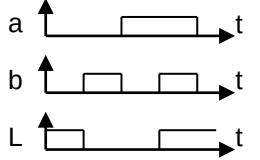
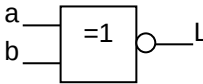
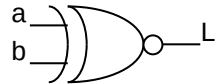


	Les fonctions logiques	UE 3 et 5
Dpt GMP	Tableau récapitulatif	CM

Fonction :	Schéma électrique :	Table de vérité :	Equation logique :	Chronogrammes :	Symbole (Norme Européenne) :	Symbole (Norme Américaine) :															
Oui		<table border="1" data-bbox="822 397 963 517"><tr><td>a</td><td>L</td></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	a	L	0	0	1	1	$L = a$												
a	L																				
0	0																				
1	1																				
Non		<table border="1" data-bbox="822 596 963 716"><tr><td>a</td><td>L</td></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	a	L	0	1	1	0	$L = \overline{a}$												
a	L																				
0	1																				
1	0																				
Et		<table border="1" data-bbox="806 788 978 984"><tr><td>a</td><td>b</td><td>L</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	a	b	L	0	0	0	0	1	0	1	0	0	1	1	1	$L = a \cdot b$			
a	b	L																			
0	0	0																			
0	1	0																			
1	0	0																			
1	1	1																			
Ou		<table border="1" data-bbox="806 1059 978 1256"><tr><td>a</td><td>b</td><td>L</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	a	b	L	0	0	0	0	1	1	1	0	1	1	1	1	$L = a + b$			
a	b	L																			
0	0	0																			
0	1	1																			
1	0	1																			
1	1	1																			

	Les fonctions logiques	UE 3 et 5
Dpt GMP	Tableau récapitulatif	CM

Fonction :	Schéma électrique :	Table de vérité :	Equation logique :	Chronogrammes :	Symbole (Norme Européenne) :	Symbole (Norme Américaine) :															
Ou exclusif		<table><tr><td>a</td><td>b</td><td>L</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	a	b	L	0	0	0	0	1	1	1	0	1	1	1	0	$L = a \oplus b$			
a	b	L																			
0	0	0																			
0	1	1																			
1	0	1																			
1	1	0																			
Non et		<table><tr><td>a</td><td>b</td><td>L</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	a	b	L	0	0	1	0	1	1	1	0	1	1	1	0	$L = \overline{a \cdot b}$			
a	b	L																			
0	0	1																			
0	1	1																			
1	0	1																			
1	1	0																			
Non ou		<table><tr><td>a</td><td>b</td><td>L</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	a	b	L	0	0	1	0	1	0	1	0	0	1	1	0	$L = \overline{a + b}$			
a	b	L																			
0	0	1																			
0	1	0																			
1	0	0																			
1	1	0																			
Non ou exclusif		<table><tr><td>a</td><td>b</td><td>L</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	a	b	L	0	0	1	0	1	0	1	0	0	1	1	1	$L = \overline{a \oplus b}$			
a	b	L																			
0	0	1																			
0	1	0																			
1	0	0																			
1	1	1																			